



I suggest using high wattage power resistors since reliability of the load is the primary consideration. Using a bunch of car tail lights in parallel would also provide a good load since chances are excellent they will not burn out at once. Here is an example for determining resistance and wattage. Suppose the maximum current I wanted to regulate was 15 Amps at 15 Volts. Since  $R = V/I$  we need a resistance of  $15 \text{ Volts}/15 \text{ Amps} = 1.0 \Omega$ . Wattage is given by  $P = IV$ .  $P = 15 \text{ Amps} * 15 \text{ Volts} = 225 \text{ Watts}$ . To be safe, I'd use 250 Watts. When hooking up your regulator make sure the system's voltage is

below 16 VDC since the NE555 is rated at a maximum 16 Volts. The regulator will regulate voltages from 12.0 to 15.8 Volts. When hooking up your shunt regulator it is a good idea to hook up the load first and make sure there are no short circuits.

**Access:**

Chris Greacen, Box 229, Reed College, Portland OR 97202

**For Power resistors:**

Hosfelt Electronics Inc. 2700 Sunset Boulevard, Steubenville, OH 43952; tel 1-800-524-6464

